

# Study of Bipolar Junction Transistor Static Characteristics

Gayatri P

2nd year, Integrated M.Sc. Physics

Roll No.: 2211185

(Dated: November 1, 2023)

In this experiment, we study the behaviour of bipolar junction transistors in two circuit configurations, namely the common emitter and the common base modes. Studying the input, output and transfer characteristics of such circuits, contributes to our understanding of transistor and transistor configurations, as well as their application in modern electronics.

## I. OBJECTIVE

- (i) To study the input and output characteristics of a PNP transistor in Common Base mode and determine transistor parameters.
- (ii) To study the input and output characteristics of an NPN transistor in Common Emitter mode and determine transistor parameters.

## II. THEORY

A Bipolar Junction Transistor, or BJT is a three terminal device having two PN-junctions connected together in series. Each terminal is given a name to identify it and these are known as the Emitter (E), Base (B) and Collector (C). There are two basic types of bipolar transistor construction, NPN and PNP, which basically describes the physical arrangement of the P-type and N-type semiconductor materials from which they are made.

Bipolar Transistors are *current amplifying* or current regulating devices that control the amount of current flowing through them in proportion to the amount of biasing current applied to their base terminal. The principle of operation of the two transistor types NPN and PNP, is exactly the same the only difference being in the biasing (base current) and the polarity of the power supply for each type.

The symbols for both the NPN and PNP bipolar transistor are shown above along with the direction of conventional current flow. The direction of the arrow in the symbol shows current flow between the base and emitter terminal, pointing from the positive P-type region to the negative N-type region, exactly the same as for the standard diode symbol. For normal operation, the emitter-base junction is forward-biased and the collector-base junction is reverse-biased.

### Transistor Configurations

There are three possible configurations possible when a transistor is connected in a circuit: (a) Common base, (b) Common emitter (c) Common collector. We will be focusing on the first two configurations in this experiment.

The behaviour of a transistor can be represented by d.c. current-voltage (I-V) curves, called the static characteristic curves of the device. The three important characteristics of a transistor are: (i) Input characteristics, (ii) Output characteristics and (iii) Transfer Characteristics. These characteristics give information about various transistor parameters, e.g. input and out dynamic resistance, current amplification factors, etc.

### A. Common Base Transistor Characteristics

In common base configuration, the base is made common to both input and output as shown in its circuit diagram.

1. **Input Characteristics:** The input characteristics is obtained by plotting a curve between  $I_E$  and  $V_{EB}$  keeping voltage  $V_{CB}$  constant. This is very similar to that of a forward-biased diode and the slope of the plot at a given operating point gives information about its input dynamic resistance.

**Input Dynamic Resistance ( $r_i$ )** is defined as the ratio of change in base emitter voltage ( $\Delta V_{EB}$ ) to the resulting change in emitter current ( $\Delta I_E$ ) at constant collector-emitter voltage ( $V_{CB}$ ). This is dynamic as its value varies with the operating cur-

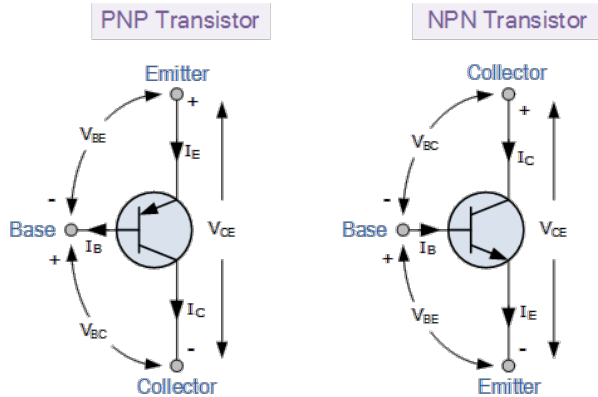


FIG. 1: Schematic diagram and conventional current flows in NPN and PNP transistors

rent in the transistor.

$$r_i = \frac{\Delta V_{EB}}{\Delta I_E} \Big|_{V_{CB}} \quad (1)$$

2. **Output Characteristics:** The output characteristic curves are plotted between  $I_C$  and  $V_{CB}$ , keeping  $I_E$  constant. The output characteristics are controlled by the input characteristics. Since  $I_C$  changes with  $I_E$ , there will be different output characteristics corresponding to different values of  $I_E$ . These curves are almost horizontal. This shows that the output dynamic resistance, defined below, is very high.

**Output Dynamic Resistance ( $r_o$ )** is defined as the ratio of change in collector-base voltage ( $\Delta V_{CB}$ ) to the change in collector current ( $\Delta I_C$ ) at a constant base current  $I_E$ .

$$r_o = \frac{\Delta V_{CB}}{\Delta I_C} \Big|_{I_E} \quad (2)$$

3. **Transfer Characteristics:** The transfer characteristics are plotted between the input and output currents ( $I_E$  versus  $I_C$ ).

**Current amplification factor ( $\alpha$ )** is defined as the ratio of the change in collector current to the change in emitter current at a constant collector-base voltage ( $V_{CB}$ ) when the transistor is in active state.

$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E} \Big|_{V_{CB}} \quad (3)$$

This is also known as small signal current gain and its value is very large. The ratio of  $I_C$  and  $I_E$  is called  $\alpha_{dc}$  of the transistor. Hence,

$$\alpha_{dc} = \frac{I_C}{I_E} \Big|_{V_{CB}} \quad (4)$$

Since  $I_C$  increases with  $I_E$  almost linearly, the values of both  $\alpha_{dc}$  and  $\alpha_{ac}$  are nearly equal.

## B. Common Emitter Transistor Characteristics

In common emitter configuration, the emitter is made common to both input and output as shown in its circuit diagram.

1. **Input Characteristics:** The variation of the base current  $I_B$  with the base-emitter voltage  $V_{BE}$  keeping the collector-emitter voltage  $V_{CE}$  fixed, gives the input characteristic in CE mode.

**Input Dynamic Resistance ( $r_i$ )** is defined as the ratio of change in base emitter voltage ( $\Delta V_{BE}$ ) to the resulting change in base current ( $\Delta I_B$ ) at constant collector-emitter voltage ( $V_{CE}$ ). This is dynamic as its value varies with the operating current in the transistor.

$$r_i = \frac{\Delta V_{BE}}{\Delta I_B} \Big|_{V_{CE}} \quad (5)$$

2. **Output Characteristics:** The variation of the collector current  $I_C$  with the collector-emitter voltage  $V_{CE}$  is called the output characteristic. The plot of  $I_C$  versus  $V_{CE}$  for different fixed values of  $I_B$  gives one output characteristic. Since the collector current changes with the base current, there will be different output characteristics corresponding to different values of  $I_B$ .

**Output Dynamic Resistance ( $r_o$ )** is defined as the ratio of change in collector-emitter voltage ( $\Delta V_{CE}$ ) to the change in collector current ( $\Delta I_C$ ) at a constant base current  $I_B$ .

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C} \Big|_{I_B} \quad (6)$$

3. **Transfer Characteristics:** The transfer characteristics are plotted between the input and output currents ( $I_B$  versus  $I_C$ ), which increase proportionately.

**Current amplification factor ( $\beta$ )** is defined as the ratio of the change in collector current to the change in base current at a constant collector-emitter voltage ( $V_{CE}$ ) when the transistor is in active state.

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \Big|_{V_{CE}} \quad (7)$$

This is also known as small signal current gain and its value is very large. The ratio of  $I_C$  and  $I_B$  is called  $\beta_{dc}$  of the transistor. Hence,

$$\beta_{dc} = \frac{I_C}{I_B} \Big|_{V_{CE}} \quad (8)$$

Since  $I_C$  increases with  $I_B$  almost linearly, the values of both  $\beta_{dc}$  and  $\beta_{ac}$  are nearly equal.

## Applications

Transistors are used in everyday life in many forms, like amplifiers and switching apparatuses. As amplifiers, they are being used in various oscillators, modulators, detectors and nearly any circuit to perform a function. In a digital circuit, transistors are used as switches.

### III. EXPERIMENTAL SETUP

#### Circuit components

1. A PNP transistor (CK100)
2. An NPN transistor (CL100)
3. Resistors (4 nos.)
4. D.C. power supply
5. Multimeters (3 nos.)
6. Connecting wires
7. Breadboard

#### Circuit Diagrams

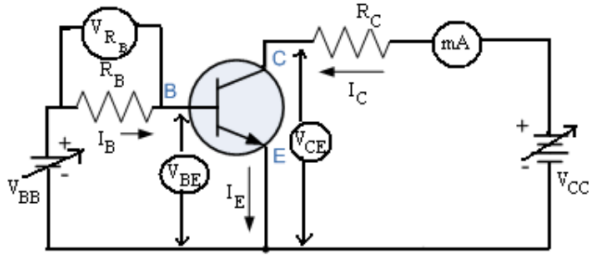


FIG. 2: NPN transistor in CE configuration

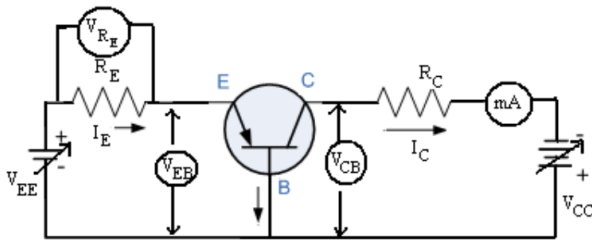


FIG. 3: PNP transistor in CB configuration

### IV. DATA ANALYSIS

#### A. CE configuration

- Transistor code: CL100 (NPN)
- $R_B = 99\text{ k}\Omega$ ,  $R_C = 993\text{ }\Omega$

#### Input Characteristics

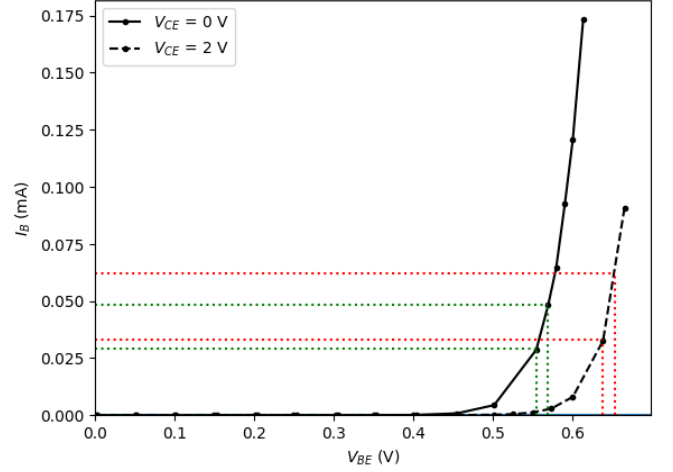


FIG. 4: Input characteristics of the NPN transistor in CE mode for different values of  $V_{CE}$

From Eq. (5), input dynamic resistance can be calculated as the inverse of slope of the I-V curve in Fig. 4. This comes out to be,

- for  $V_{CE} = 0\text{ V}$ ,  $r_i = 769.23\text{ }\Omega$
- for  $V_{CE} = 2\text{ V}$ ,  $r_i = 517.24\text{ }\Omega$

#### Output Characteristics

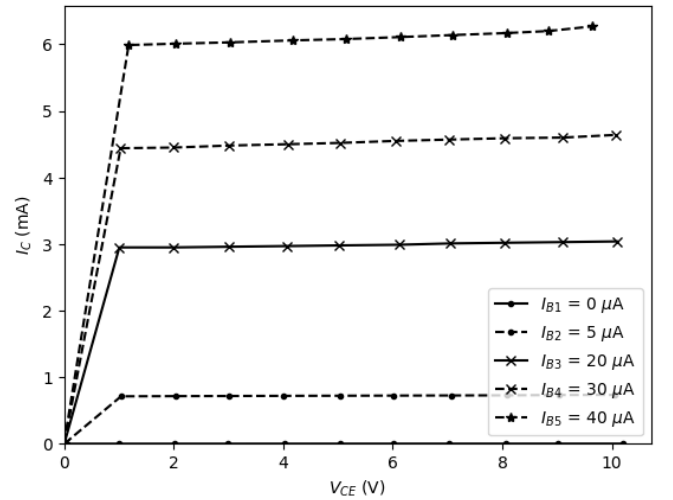


FIG. 5: Output characteristics of the NPN transistor in CE mode for different values of  $I_B$

From Eq. (6), output dynamic resistance can be calculated as the inverse of slope of the I-V curve in the active region of the plot in Fig. 5. This comes out to be,

- for  $I_B = 0 \mu\text{A}$ ,  $r_o = 8019.39 k\Omega$
- for  $I_B = 5 \mu\text{A}$ ,  $r_o = 399.89 k\Omega$
- for  $I_B = 20 \mu\text{A}$ ,  $r_o = 101.00 k\Omega$
- for  $I_B = 30 \mu\text{A}$ ,  $r_o = 50.47 k\Omega$
- for  $I_B = 40 \mu\text{A}$ ,  $r_o = 36.47 k\Omega$

The high magnitudes of  $r_o$  is due to the reverse biased state of the base-collector diode, in the active state.

### Transfer Characteristics

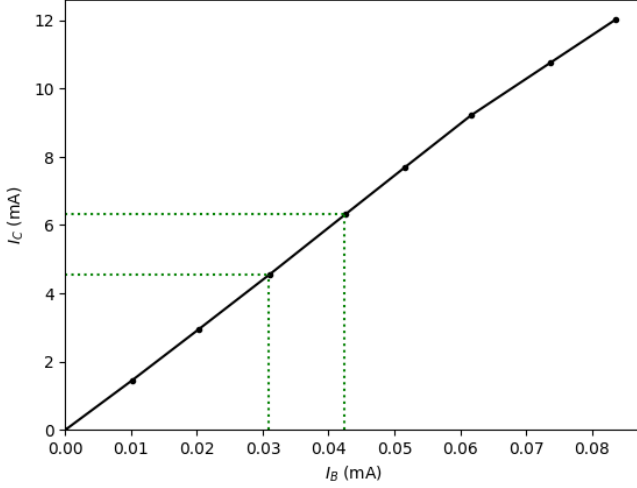


FIG. 6: Transfer characteristics of the NPN transistor in CE mode for a fixed  $V_{CE} = 1 \text{ V}$

From Eq. (7), the current amplification factor can be calculated from as the slope of the  $I_C$  vs  $I_B$  curve in Fig. 6. This comes out to be  $\beta_{ac} = 154.78$ . Since the plot is linear, the value of  $\beta_{dc}$  (from Eq. (8)) can also said to be equal to 154.78.

### B. CB configuration

- Transistor code: CK100 (PNP)
- $R_E = R_C = 151.1 \Omega$

### Input Characteristics

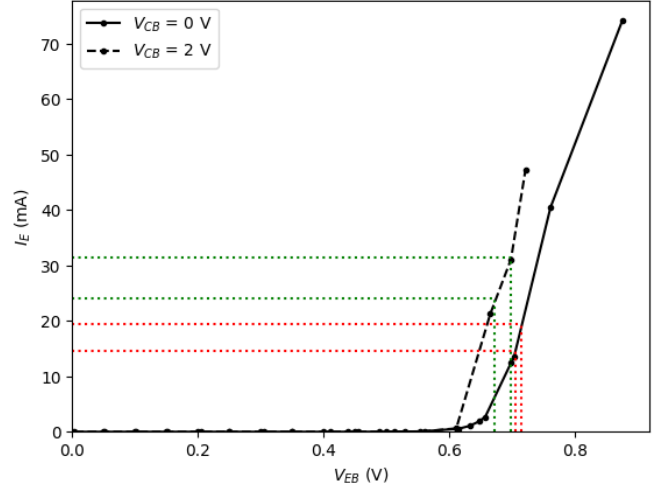


FIG. 7: Input characteristics of the PNP transistor in CB mode for different values of  $V_{CB}$

From Eq. (1), input dynamic resistance can be calculated as the inverse of slope of the I-V curve in Fig. 7. This comes out to be,

- for  $V_{CB} = 0 \text{ V}$ ,  $r_i = 3.51 \Omega$
- for  $V_{CB} = 2 \text{ V}$ ,  $r_i = 2.13 \Omega$

### Output Characteristics

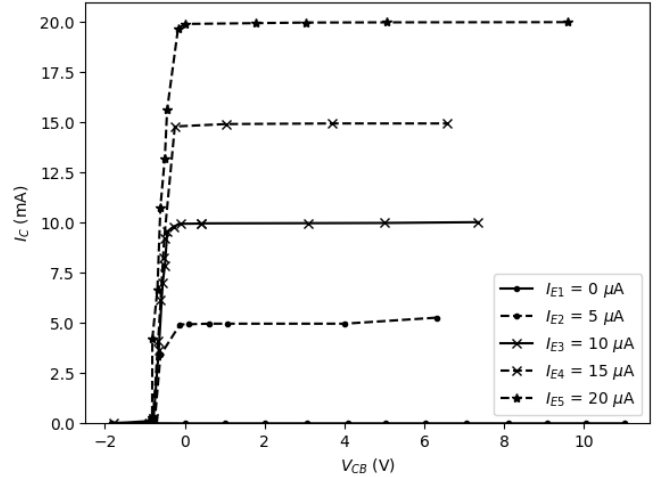


FIG. 8: Output characteristics of the PNP transistor in CB mode for different values of  $I_E$

From Eq. (2), output dynamic resistance can be calculated as the inverse of slope of the I-V curve in the active region of the plot in Fig. 8. This comes out to be,

- for  $I_E = 0 \mu\text{A}$ ,  $r_o = 9700.00 k\Omega$
- for  $I_E = 5 \mu\text{A}$ ,  $r_o = 18.97 k\Omega$
- for  $I_E = 10 \mu\text{A}$ ,  $r_o = 192 k\Omega$
- for  $I_E = 15 \mu\text{A}$ ,  $r_o = 88.33 k\Omega$
- for  $I_E = 20 \mu\text{A}$ ,  $r_o = 202.70 k\Omega$

### Transfer Characteristics

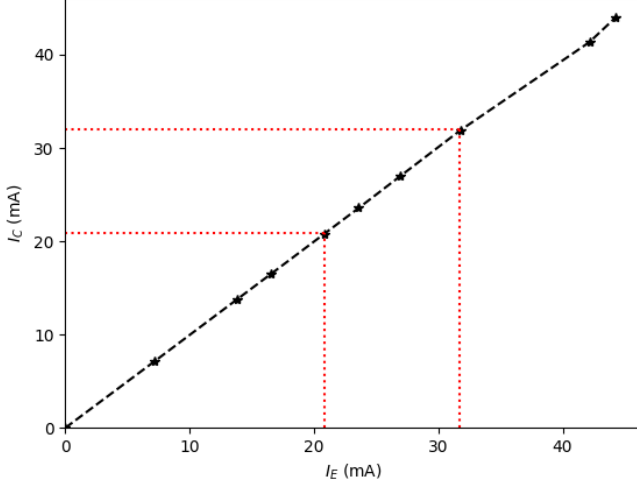


FIG. 9: Transfer characteristics of the PNP transistor in CB mode for a fixed  $V_{CB} = 1 \text{ V}$

From Eq. (3), the current amplification factor can be calculated from as the slope of the  $I_C$  vs  $I_E$  curve in Fig. 6. This comes out to be  $\alpha_{ac} = 1.02$ . Since the plot is linear, the value of  $\alpha_{dc}$  (from Eq. (4)) can also said to be equal to 1.02.

## V. RESULTS AND DISCUSSION

We have successfully constructed CE and CB modes using a NPN and PNP transistor respectively. From analysing voltage and current in the circuit, we were able to study the following characteristics.

### For an NPN transistor in CE mode

From Fig. 4, we can observe that when the input voltage  $V_{BE}$  is increased initially there is no current produced, further when it is increased the input current  $I_B$  increases steeply. When the output voltage  $V_{CE}$  is further increased the curve shifts right side, i.e., higher value of  $V_{BE}$  is required to activate the transistor.

The output characteristics show that initially for very small values of  $V_{CE}$ ,  $I_C$  increases almost linearly. When  $V_{CE}$  is more than that required to reverse bias the base-collector junction,  $I_C$  increases very little with  $V_{CE}$ .

Here by plotting  $I_C$  vs  $V_{CE}$  for fixed values of  $I_B$ , (Fig. 5) we can see that, for a fixed value of  $V_{CE}$ ,  $I_B$  increases with  $I_C$ .

Furthermore, the current amplification factor was found to be,  $\beta = 154.78$ .

### For a PNP transistor in CB mode

From Fig. 7, we can observe that when the input voltage  $V_{EB}$  is increased initially there is no current produced, further when it is increased the input current  $I_E$  increases steeply. When the output voltage  $V_{CB}$  is further increased the curve shifts left side, i.e., lower value of  $V_{EB}$  is required to activate the transistor.

Furthermore, output characteristics show that initially for very small values of  $V_{CB}$ ,  $I_C$  increases almost linearly. When  $V_{CB}$  is more than that required,  $I_C$  increases very little with  $V_{CB}$ . We can also see that the maximum value  $I_C$  increases with  $I_E$ .

The current amplification factor, was found to be  $\alpha = 1.02$ .

## VI. PRECAUTIONS

1. Verify that the multimeters are in working condition before starting the experiment.
2. Switch on the circuit only after verifying the connections to be proper.
3. Do not change the any components on the circuit while the circuit is switched on.

---

[1] SPS. Lab manual. Website, 2023. [https://www.niser.ac.in/sps/sites/default/files/6\\_Transistor%20characteristics.pdf](https://www.niser.ac.in/sps/sites/default/files/6_Transistor%20characteristics.pdf).